

Simulation # 7

Two port network – Z Parameters



Electrical Network Simulation Laboratory (EE2701)
Department of Electrical Engineering,
NIT Rourkela

Aim of the Expt.:

- Understand two port circuits
- Calculate Z parameters for two port networks
- Use Multisim to find the Z parameters for given circuit

Theory:

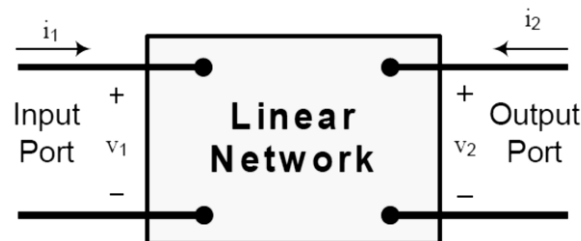


Figure 1 Generalisation of two port network

There are six groups of two-port circuit parameters (e.g., the impedance z-parameters, admittance y-parameters, hybrid h-parameters, etc) that can be used to relate the input/output voltage & current variables. Any set of parameters can be derived from the other ones.

The z-parameters are defined by:

$$\begin{aligned} V_1 &= Z_{11} I_1 + Z_{12} I_2 \\ V_2 &= Z_{21} I_1 + Z_{22} I_2 \end{aligned}$$

These parameters can be measured by the following tests (based on open-circuit input port condition, and open-circuit output port condition):

$$\begin{aligned} Z_{11} &= V_1 / I_1 \text{ when } I_2 = 0 \\ Z_{12} &= V_1 / I_2 \text{ when } I_1 = 0 \\ Z_{21} &= V_2 / I_1 \text{ when } I_2 = 0 \\ Z_{22} &= V_2 / I_2 \text{ when } I_1 = 0 \end{aligned}$$

Circuit:

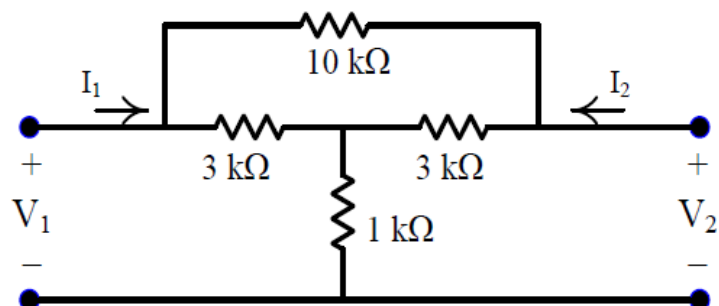


Figure 2 Circuit for experiment

Simulation:

1. Build the circuit of Figure 2 in Multisim Electronics Workbench.
2. Apply a DC voltage test source to the input port with the output port open. Use a voltmeter and ammeter to read the values of the voltages and currents necessary to compute Z_{11} and Z_{21} . Observe the proper polarity of the currents.
3. Repeat a similar procedure with a DC voltage test source applied to the output port with the input port open. Use a voltmeter and ammeter to read the voltage and current values, and derive the parameters Z_{22} and Z_{12} .
4. Record the values of the Z-parameters in Table 1.

Table 1 Z-parameters for circuit 1

Z-parameters	Z ₁₁	Z ₁₂	Z ₂₁	Z ₂₂
Simulation				
Calculation				

Questions:

1. Explain whether this two-port circuit is reciprocal, and why?
2. Explain whether this two-port circuit is symmetric, and why?
3. Run the simulation for a loaded two port network as shown in Figure 3 and find the voltage and current gain. $V_s = 10$ V DC, $G_v = V_2/V_s$ and current gain $G_i = I_2/I_1$.

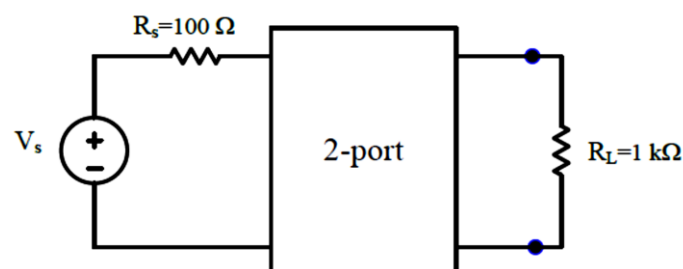


Figure 3 Loaded two-port network